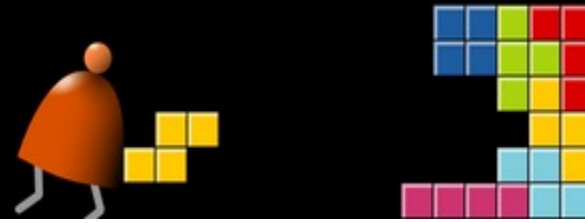


From Nand to Tetris

Building a Modern Computer from First Principles



Chapter 3

Memory


These slides support chapter 3 of the book

The Elements of Computing Systems

By Noam Nisan and Shimon Schocken

MIT Press, 2021

Nand to Tetris Roadmap: Hardware

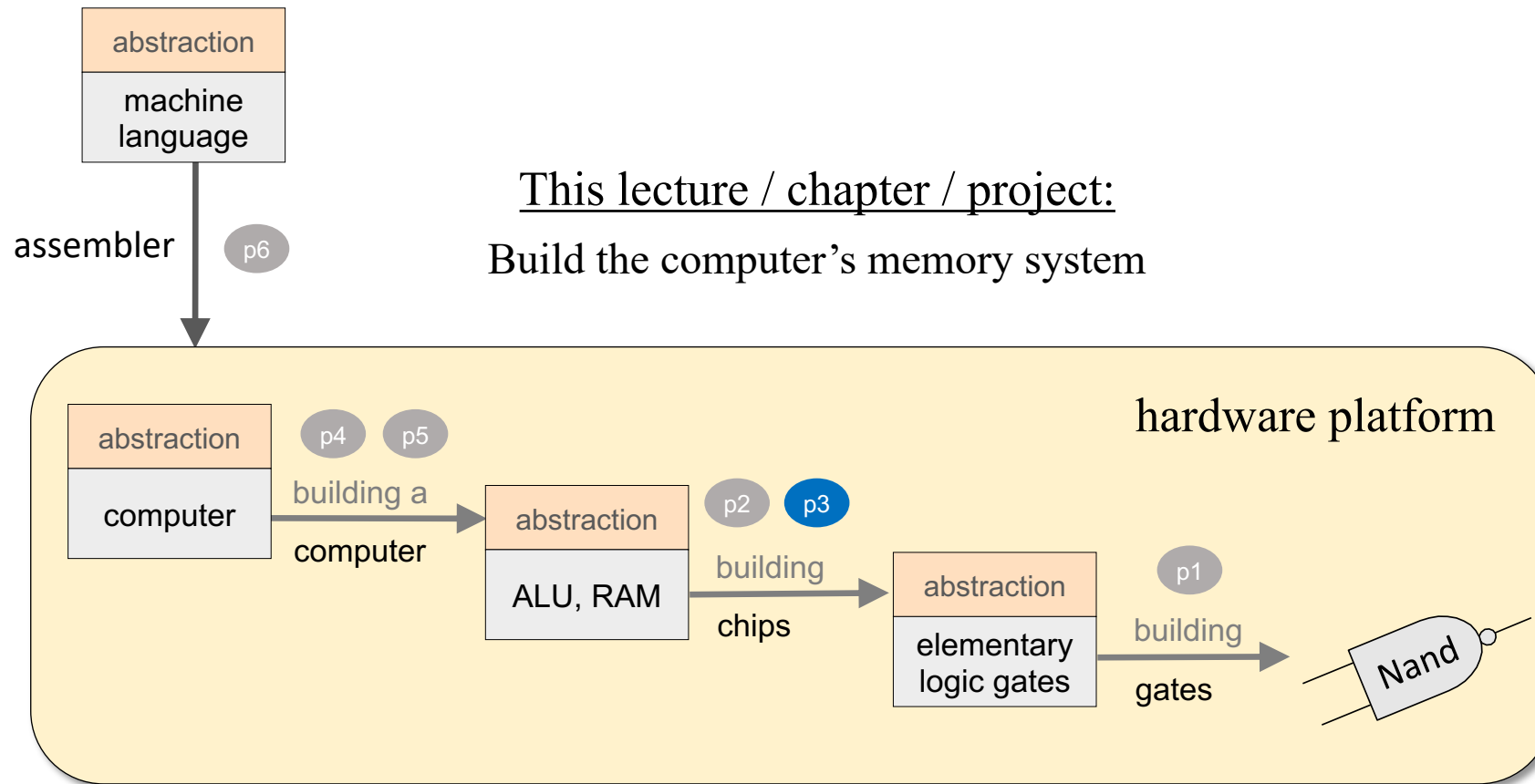

This lecture / chapter / project:
Build the computer's memory system

Project 1: Build basic logic gates

Project 2: Build the ALU

A common theme in computer science

- We articulate a simple model (the simpler, the better)
- We explore the model's power:
 - What it can do
 - What it cannot do
- We then extend the model, making it more powerful

Case in point:

Logic gates.

Logic gates

Model: And, Or, Not, ...

- Simple, and powerful:
Logic gates can realize any Boolean function, and can be combined to form very useful artifacts, like an ALU
- But, as a *practical model of computation*, logic gates fall short

Some limitations


- Logic gates cannot store information (bits) over time
- Feedback loops are not allowed: A chip's output cannot serve as its input
- Logic gates can handle only inputs of a fixed size.
For example, we can build an Or3 gate, and an Or4 gate, and so on, but we cannot build a single gate that computes Or for any given number of inputs

Extension

Allow logic gates to be sensitive to the progression of *time*.

Time-independent logic

 - So far we ignored *time*
- The chip's inputs were just “sitting there” – fixed and unchanging
- The chip's output was a function (“combination”) of the current inputs, and the current inputs only
- This style of gate logic is called:
 - *time-independent logic*
 - *combinational logic*
- All the chips that we discussed and developed so far were combinational



ALU: The “topmost”
combinational chip

Hello, time

Software needs:

- The hardware must be able to remember things, over time:
- The hardware must be able to do things, one at a time (sequentially):

Example (variables):


x = 17

Example (iteration):

```
for i in range(0, 10):  
    print(i)
```

Hardware needs:

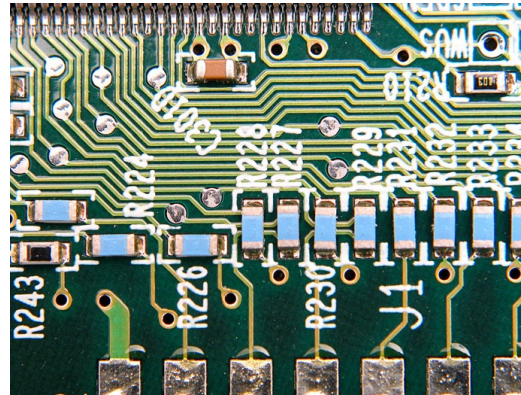- The hardware must handle the *physical time delays* associated with *computing* and *moving* data from one chip to another.



Hello, time

Software needs:

- The hardware must be able to remember things, over time:
- The hardware must be able to do things, one at a time (sequentially):

Example (variables):

```
x = 17
```


Example (iteration):

```
for i in range(0, 10):  
    print(i)
```

Hardware needs:


- The hardware must handle the *physical time delays* associated with *computing* and *moving* data from one chip to another.

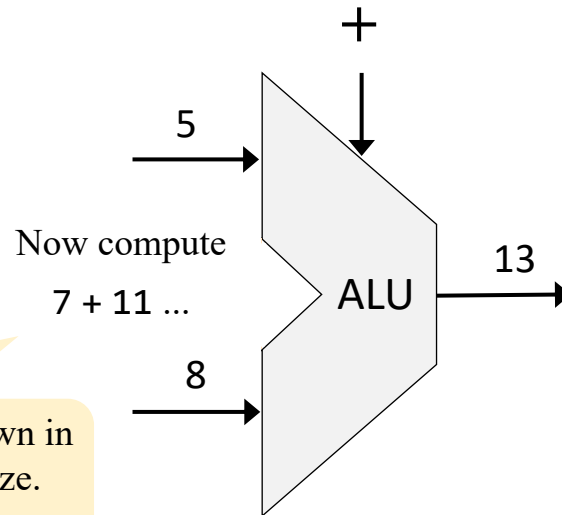It will take some time before 7 and 11 will settle down in the input pins, and before the sum $7 + 11$ will stabilize. Till then, the ALU will output nonsense.



Hello, time

 Solution: We can neutralize the time delays if we decide to use *discrete time*



- Set the *cycle length* to be slightly $>$ than the maximum time delay, and...
- Decide to use the chips' outputs only at the end of cycles (time-steps), ignoring what happens within cycles
- Details later.

Memory

Memory: The faculty of the brain by which data or information is encoded, stored, and retrieved when needed.

It is the *retention of information over time* for the purpose of influencing future action (Wikipedia)

Memory is time-based:


We remember *now* what was committed to memory *earlier*.



*It's a poor sort of memory
that only works backwards.*


-Lewis Carroll, through the White Queen

Memory

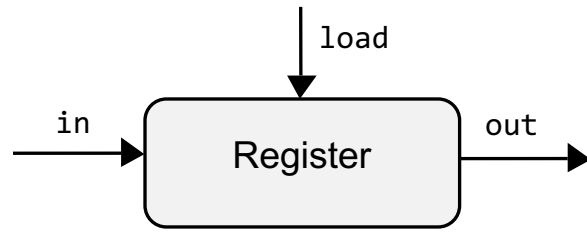

Basic operations:

- “Loading” a value
- “Storing” a value

 

loading

storing

$x = 21, 21, 21, 21, 21, 21, 21, \dots$

loading

storing

The challenge: Building chips that realize this functionality,
Chips that can *change and maintain state*.

Chapter 3: Memory

Abstraction

- Representing time
- Clock
- Registers
- RAM
- Counters

Implementation

- Data Flip Flop
- Registers
- RAM
- Project 3: Chips
- Project 3: Guidelines

Chapter 3: Memory

Abstraction


 Representing time

- Clock
- Registers
- RAM
- Counters

Implementation

- Data Flip Flop
- Registers
- RAM
- Project 3: Chips
- Project 3: Guidelines

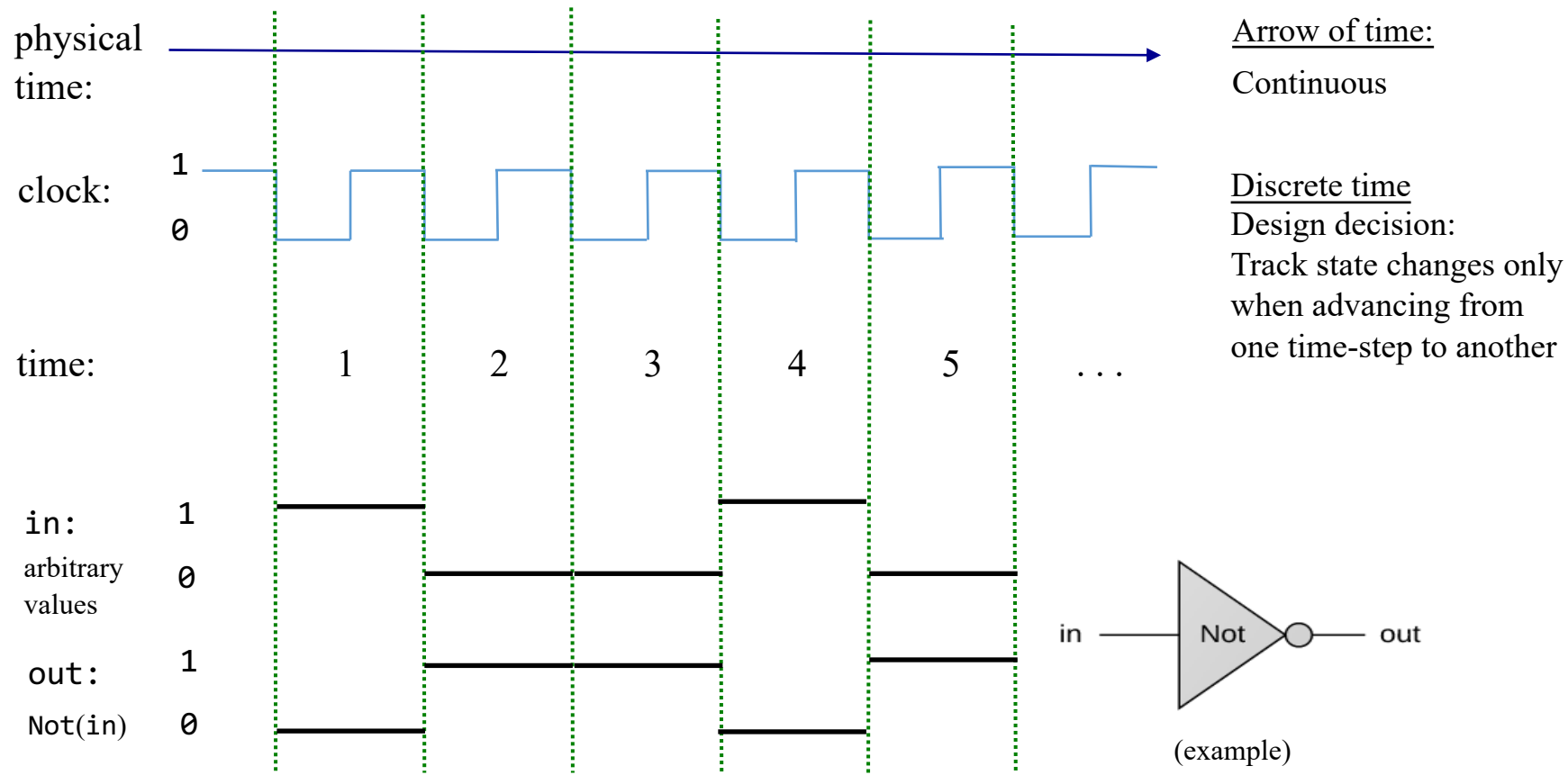
Chip behavior over time (example: Not gate)



Desired / idealized behavior of the in and out signals:


That's how we *want* the hardware to behave

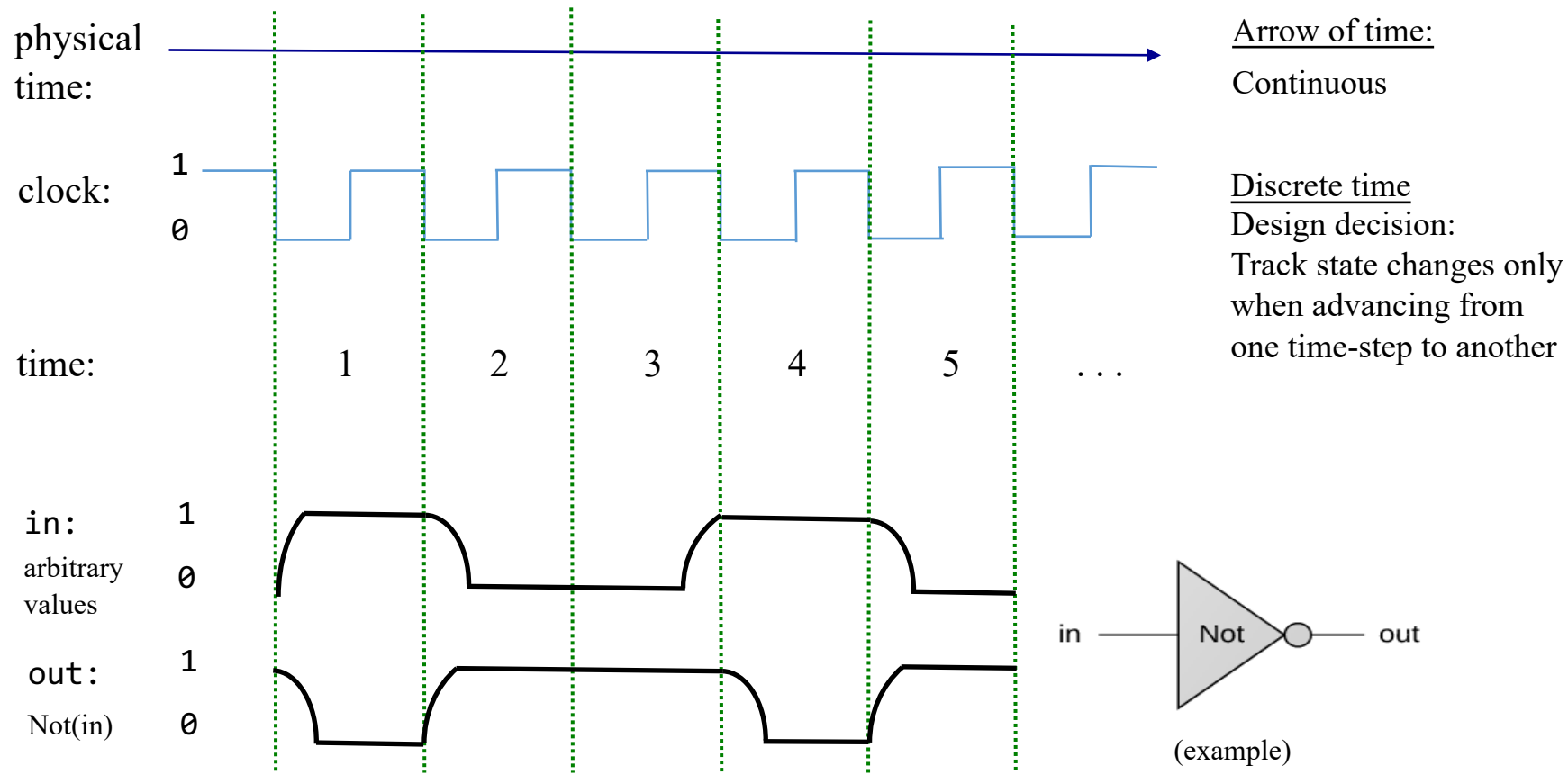Chip behavior over time (example: Not gate)




Actual behavior of the in and out signals:
Influenced by physical time delays

 Chip behavior over time (example: Not gate)



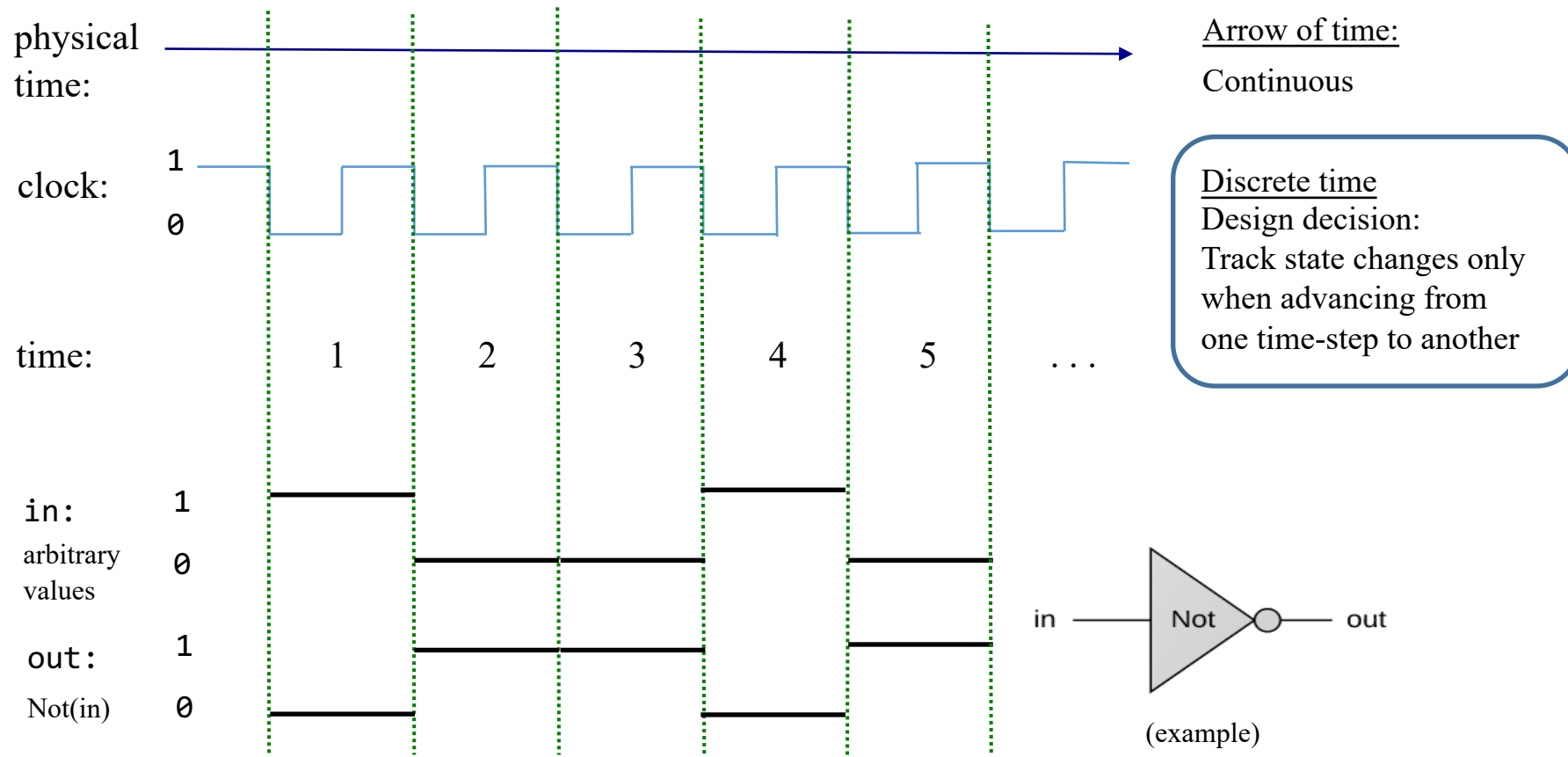Chip behavior over time (example: Not gate)



Resulting effect:

- Combinational chips react “immediately” to their inputs
- Facilitated by the decision to track changes only at cycle ends

Chapter 3: Memory

Abstraction

✓ Representing time


➡ Clock

- Registers
- RAM
- Counters


Implementation

- Data Flip Flop
- Registers
- RAM
- Project 3: Chips
- Project 3: Guidelines

Clock

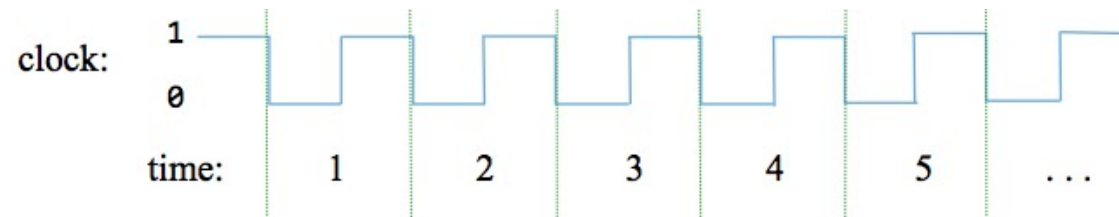

Clock: Simulated implementation

 

Interactive simulation

A clock icon, used to generate a sequence of tick-tock signals:

0, 0+, 1, 1+, 2, 2+, 3, 3+, ...




Script-based simulation

“tick” and “tock” commands,
used to advance the clock:

```
...  
// Sets inputs, advances the clock, and  
// writes output values as it goes along.  
set in 19,  
set load 1,  
tick,  
output,  
tock,  
output,  
tick, tock,  
output,  
...
```


Clock: Physical implementation

 

Physical clock

An *oscillator* is used to deliver an ongoing train of “tick/tock” signals

 “1 MHz electronic oscillator circuit which uses the resonant properties of an internal quartz crystal to control the frequency. Provides the clock signal for digital devices such as computers.” (Wikipedia)



Chip diagram convention:
A triangle icon represents a clock signal input

The oscillator’s output signal is fed to all the time-based (clocked) chips in the computer

Chapter 3: Memory

Abstraction

✓ Representing time

✓ Clock

➡ Registers

- RAM
- Counters

Implementation


- Data Flip Flop
- Registers
- RAM
- Project 3: Chips
- Project 3: Guidelines

Combinational logic / Sequential logic

Combinational logic:

The output depends on the current inputs


The clock is used to stabilize outputs

 

Sequential logic:


The output depends on:

 - Previous inputs
- Current inputs (optionally)





This behavior can be used to build chips designed to maintain state: **Registers**.

Registers

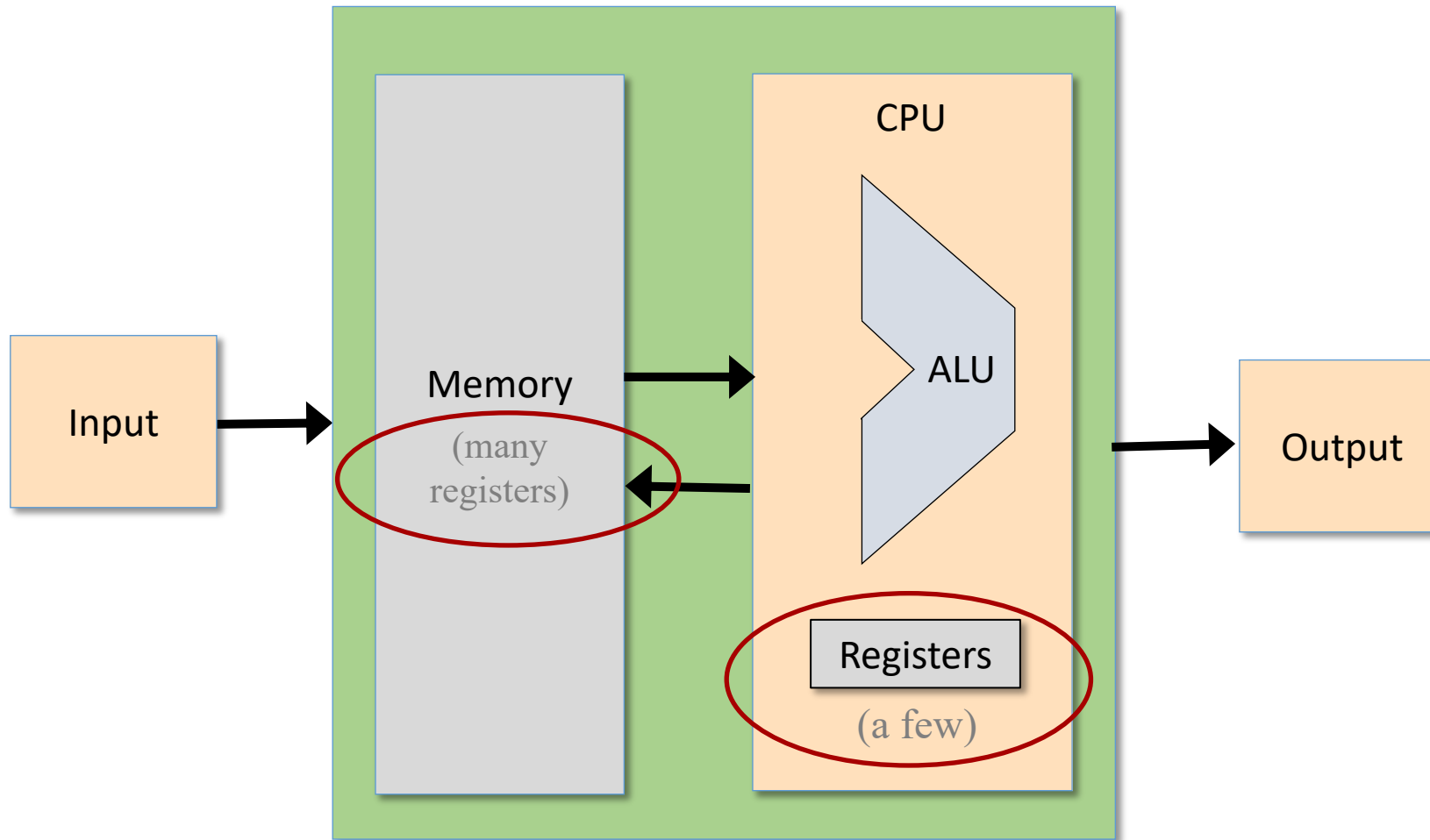

Computer Architecture

Registers

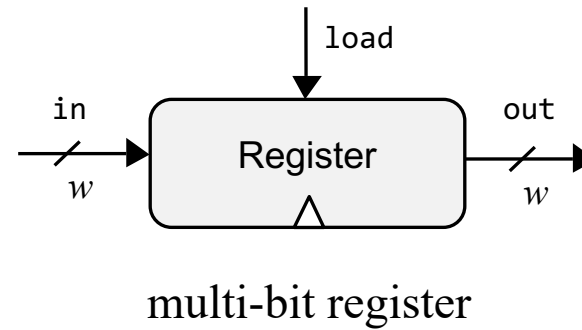 

Designed to:

- “Store” a value , until...
- “Loaded” with a new value

time:

$x = 17, 17, 17, 17, 17, 17, 17, 17, \dots, 17$

loading


storing

$x = 21, 21, 21, 21, 21, 21, \dots, 21$

loading

storing


1-Bit register

 


1-Bit register

```
if load( $t$ ) then  
    out( $t + 1$ ) = in( $t$ )  
else  
    out( $t + 1$ ) = out( $t$ )
```


1-Bit register

 

 
if $\text{load}(t)$ then
 $\text{out}(t+1) = \text{in}(t)$
else
 $\text{out}(t+1) = \text{out}(t)$




1-Bit register

 

 
if $\text{load}(t)$ then
 $\text{out}(t+1) = \text{in}(t)$
else
 $\text{out}(t+1) = \text{out}(t)$




1-Bit register

 

 
if $\text{load}(t)$ then
 $\text{out}(t+1) = \text{in}(t)$
else
 $\text{out}(t+1) = \text{out}(t)$




1-Bit register

 

 
if $\text{load}(t)$ then
 $\text{out}(t+1) = \text{in}(t)$
else
 $\text{out}(t+1) = \text{out}(t)$




1-Bit register

 

 
if $\text{load}(t)$ then
 $\text{out}(t+1) = \text{in}(t)$
else
 $\text{out}(t+1) = \text{out}(t)$




1-Bit register

 

 
if $\text{load}(t)$ then
 $\text{out}(t+1) = \text{in}(t)$
else
 $\text{out}(t+1) = \text{out}(t)$




1-Bit register

 

 
if $\text{load}(t)$ then
 $\text{out}(t+1) = \text{in}(t)$
else
 $\text{out}(t+1) = \text{out}(t)$




1-Bit register

 

 
if $\text{load}(t)$ then
 $\text{out}(t+1) = \text{in}(t)$
else
 $\text{out}(t+1) = \text{out}(t)$




1-Bit register

 

 if $\text{load}(t)$ then
 $\text{out}(t+1) = \text{in}(t)$
else
 $\text{out}(t+1) = \text{out}(t)$



1-Bit register

 

```
if load( $t$ ) then
  out( $t + 1$ ) = in( $t$ )
else
  out( $t + 1$ ) = out( $t$ )
```

Usage:

To read:


probe out (out always emits the register's state)

To write:

set in = v
set load = 1 Result: The register's state becomes v ;
From the next time-step onward, out will emit v .

Best practice: Following writing, set load to 0

Multi-bit register

 

We'll focus on bit width $w = 16$,
without loss of generality

Load / store behavior: Exactly the same as a 1-Bit register

Read / write usage: Exactly the same as a 1-Bit register



Chapter 3: Memory

Abstraction

✓ Representing time

✓ Clock

✓ Registers


➡ RAM

- Counters


Implementation

- Data Flip Flop
- Registers
- RAM
- Project 3: Chips
- Project 3: Guidelines

Computer architecture

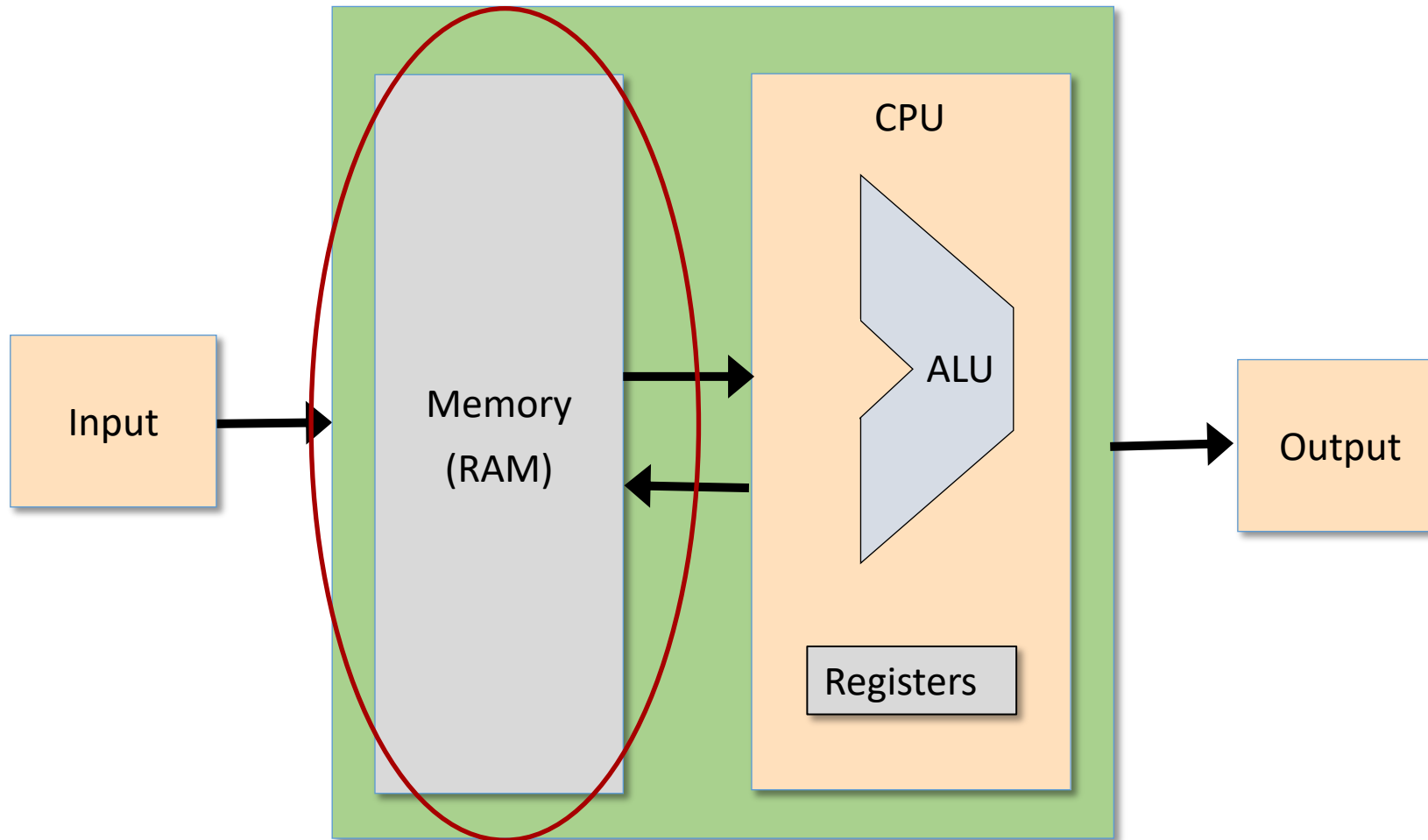

RAM

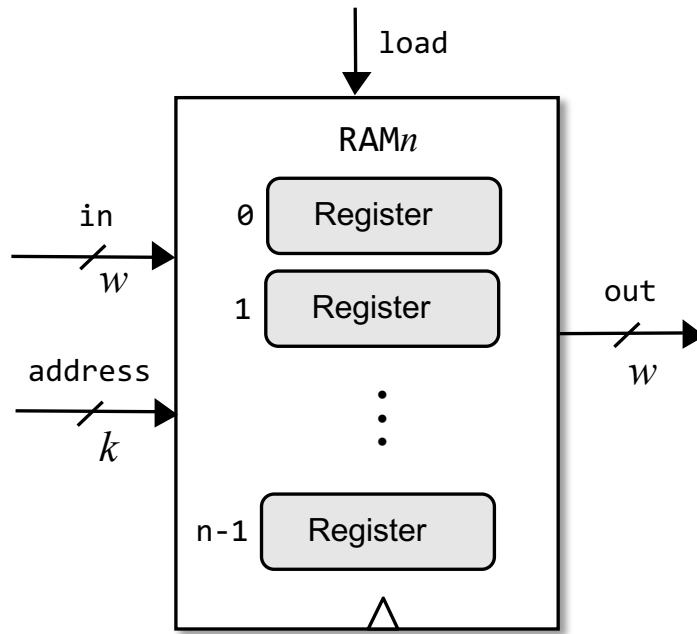

Practice question:

Suppose that the RAM size $n = 8$ registers.

What should be the value of k ?


Answer:

$$k = \log_2 n$$

Abstraction: A sequence of n addressable, w -bit registers

Word width: Typically $w = 16, 32, 64$ bits (Hack computer: $w = 16$)

RAM

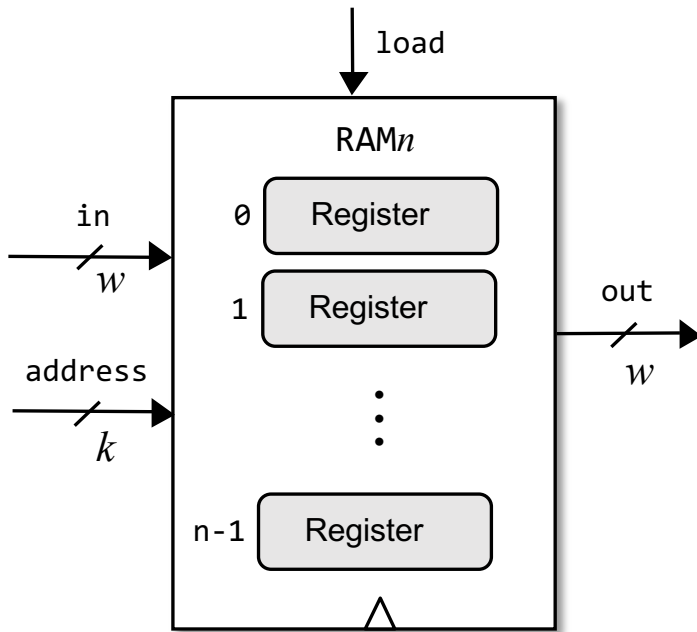

Why “Random Access Memory”?

Irrespective of the RAM size (n), every randomly selected register can be accessed “instantaneously”, at more or less the same speed.



Chapter 3: Memory

Abstraction

✓ Representing time

✓ Clock

✓ Registers


✓ RAM

➡ Counters

Implementation

- Data Flip Flop
- Registers
- RAM
- Project 3: Chips
- Project 3: Guidelines

RAM

 

Behavior

If $\text{load} == 0$, the RAM maintains its state

If $\text{load} == 1$, $\text{RAM}[\text{address}]$ is set to the value of in

The loaded value will be emitted by out from the next time-step (cycle) onward, until the next load

(Only one RAM register is selected;
All the other registers are not affected)

Usage: **To read register i :**

set $\text{address} = i$,

probe out (out always emits the value of $\text{RAM}[i]$)

To write v in register i :

set $\text{address} = i$,


set $\text{in} = v$,

set $\text{load} = 1$

Result: $\text{RAM}[i] \leftarrow v$

From the next time-step onward
out will emit v

Computer architecture

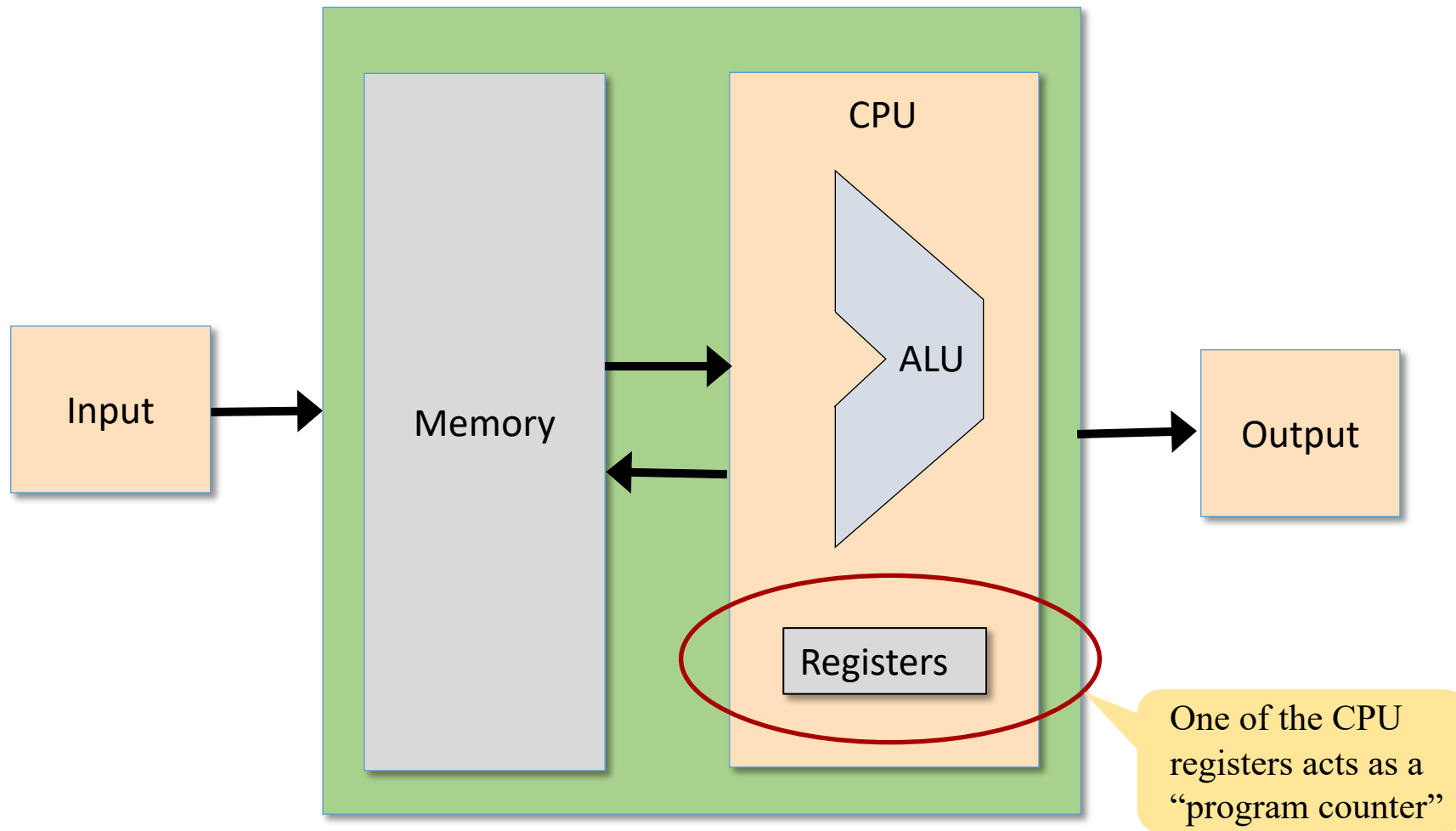

Counter

- Later in the course we will see that the computer keeps track of which instruction should be fetched and executed next
- This task is regulated by a register typically called Program Counter
- The PC stores the address of the instruction that should be fetched and executed next
- Three basic PC operations:

Reset: fetch the first instruction

PC = 0


Next: fetch the next instruction

PC++

Goto: fetch instruction n

PC = n

Counter

 

if $\text{reset}(t)$	$\text{out}(t+1) = 0$
else if $\text{load}(t)$	$\text{out}(t+1) = \text{in}(t)$
else if $\text{inc}(t)$	$\text{out}(t+1) = \text{out}(t) + 1$
else	$\text{out}(t+1) = \text{out}(t)$

Usage:

To read:

probe out

To set:

set in to v ,
assert load,
set the other control bits to 0

To reset:

assert reset,
set the other control bits to 0

To count:

assert inc,
set the other control bits to 0



Chapter 3: Memory

Abstraction

- Representing time
- Clock
- Registers
- RAM
- Counters

Implementation

- Data Flip Flop
- Registers
- RAM
- Project 3: Chips
- Project 3: Guidelines



Chapter 3: Memory

Abstraction

- Representing time
- Clock
- Registers
- RAM
- Counters

Implementation





- Data Flip Flop
- Registers
- RAM
- Project 3: Chips
- Project 3: Guidelines

DFF

Data Flip Flop (aka *latch*)

 
 
The most elementary sequential gate: Outputs the input in the previous time-step



DFF

Data Flip Flop (aka *latch*)

 
 
The most elementary sequential gate: Outputs the input in the previous time-step



DFF

Data Flip Flop (aka *latch*)

 
 
The most elementary sequential gate: Outputs the input in the previous time-step



DFF

Data Flip Flop (aka *latch*)

 
 
The most elementary sequential gate: Outputs the input in the previous time-step



DFF

Data Flip Flop (aka *latch*)

 
 
The most elementary sequential gate: Outputs the input in the previous time-step



DFF

Data Flip Flop (aka *latch*)

 
 
The most elementary sequential gate: Outputs the input in the previous time-step



DFF

Data Flip Flop (aka *latch*)

 
 
The most elementary sequential gate: Outputs the input in the previous time-step



DFF

Data Flip Flop (aka *latch*)

 
 
The most elementary sequential gate: Outputs the input in the previous time-step



From DFF to a 1-Bit register


Data Flip Flop (aka *latch*)

  The most elementary sequential gate: Outputs the input in the previous time-step




How can we “load” and then “maintain” a value (0 or 1) over time, without having to feed the value in every cycle?

From DFF to a 1-Bit register

 

We have to realize a “loading” behavior and a ”storing” behavior, and be able to select between these two states

From DFF to a 1-Bit register

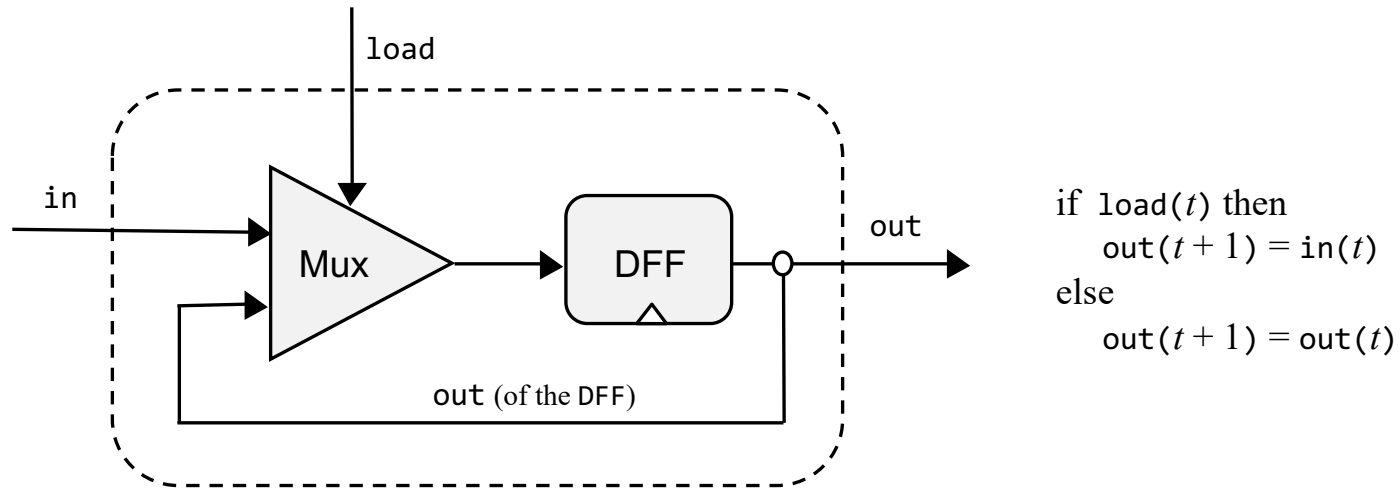


if $\text{load}(t)$ then
 $\text{out}(t+1) = \text{in}(t)$
else
 $\text{out}(t+1) = \text{out}(t)$

We have to realize a “loading” behavior and a ”storing” behavior,
and be able to select between these two states

Behavior

if $\text{load} == 1$ the register’s value becomes in
else the register maintains its current value

From DFF to a 1-Bit register

 


Behavior

if $\text{load} == 1$ the register's value becomes in
else the register maintains its current value

Register

1-Bit register

Stores one bit
over time

 

zoom out...

```
if load(t) then
  out(t + 1) = in(t)
else
  out(t + 1) = out(t)
```


Behavior

```
if load == 1  the register's value becomes in
else          the register maintains its current value
```

Register

1-Bit register


Stores one bit
over time

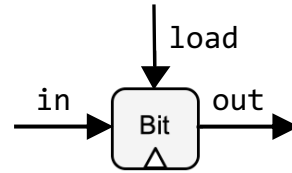

if $\text{load}(t)$ then
 $\text{out}(t+1) = \text{in}(t)$
else
 $\text{out}(t+1) = \text{out}(t)$

w-bit Register

Stores w bits
over time

 

Behavior




if $\text{load} == 1$ the register's value becomes in
else the register maintains its current value

Chapter 3: Memory


Abstraction

- Representing time
- Clock
- Registers
- RAM
- Counters


Implementation

-  Data Flip Flop
-  Registers
-  RAM
 - Project 3: Chips
 - Project 3: Guidelines

Memory hierarchy

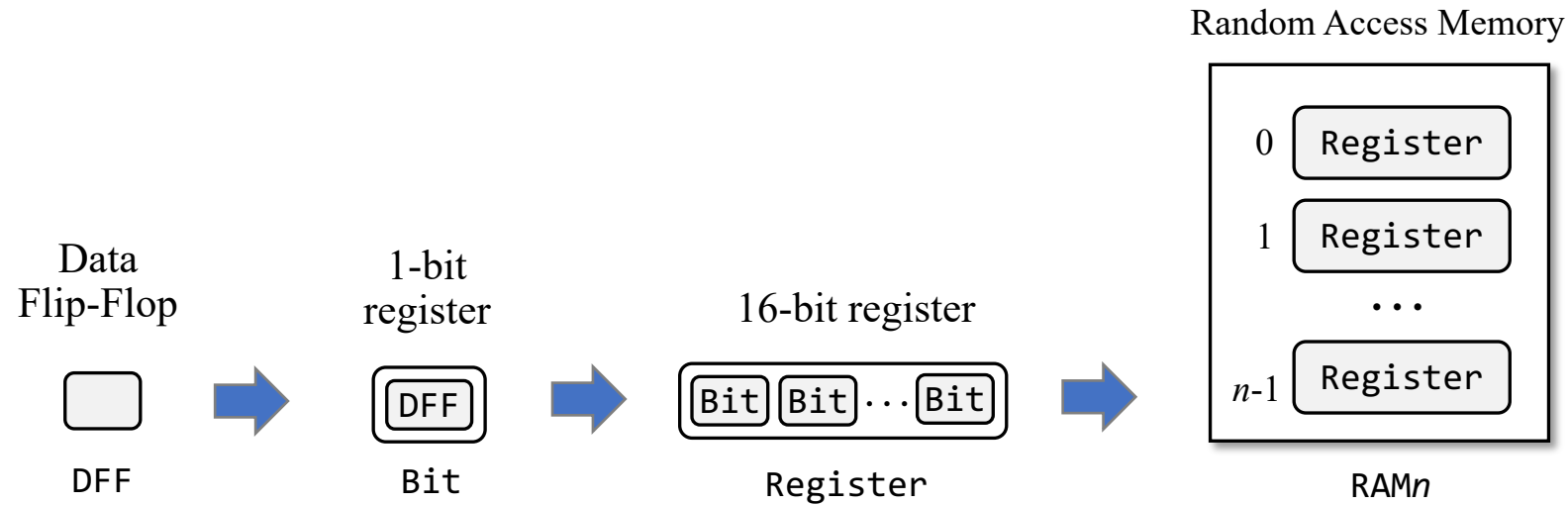


Memory hierarchy

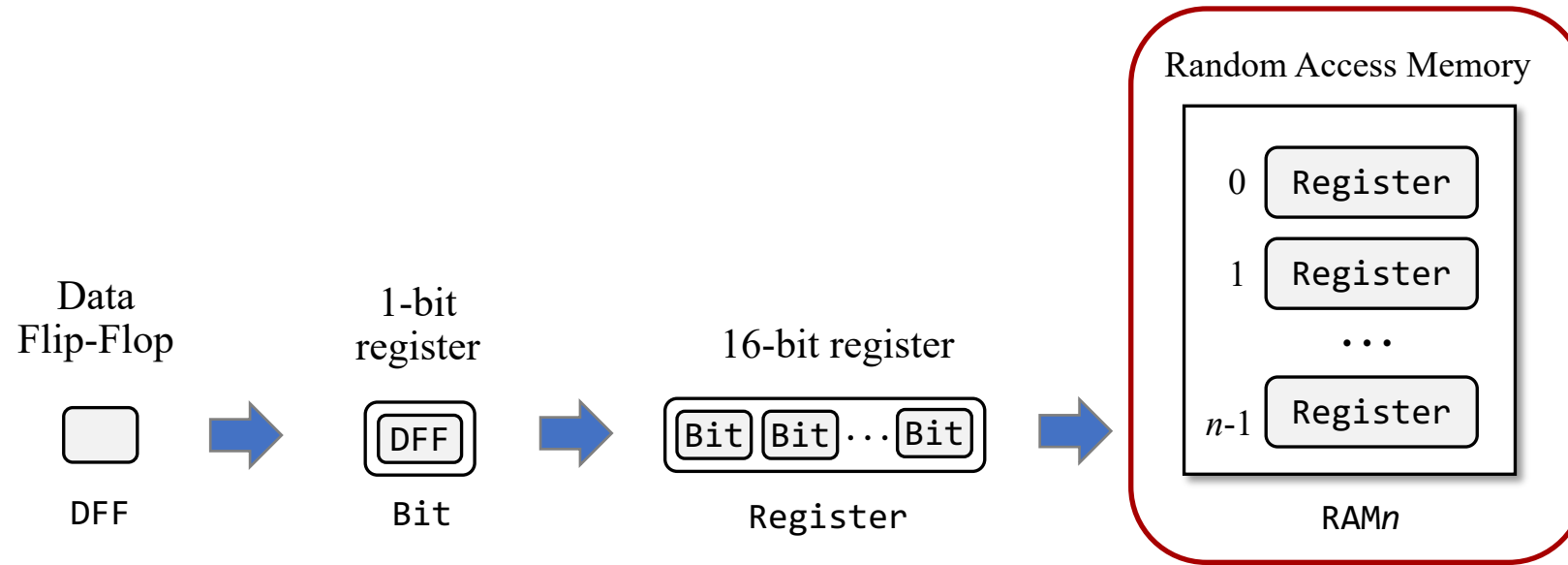

RAM: Abstraction

RAM of n
registers:

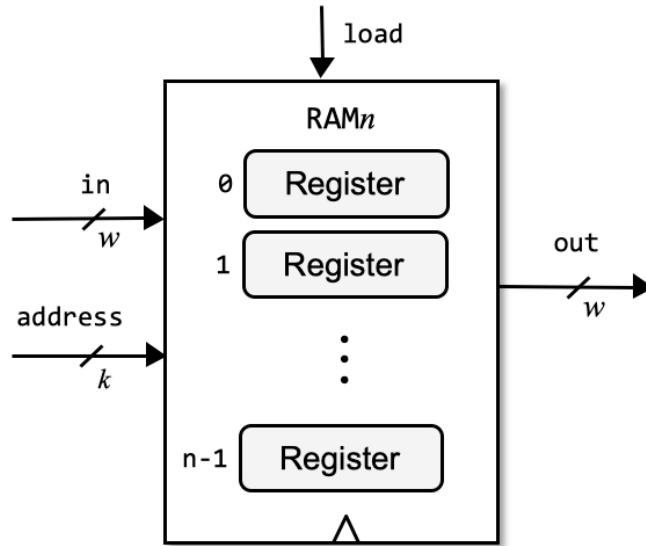


Usage: **To read register i :**
 set address = i ,
 probe out (out always emits the state of $RAM[i]$)

To write v in register i :
 set address = i ,
 set in = v , Result: $RAM[i] \leftarrow v$
 set load = 1 From the next time-step onward, out emits v

RAM: Implementation


RAM of n registers:

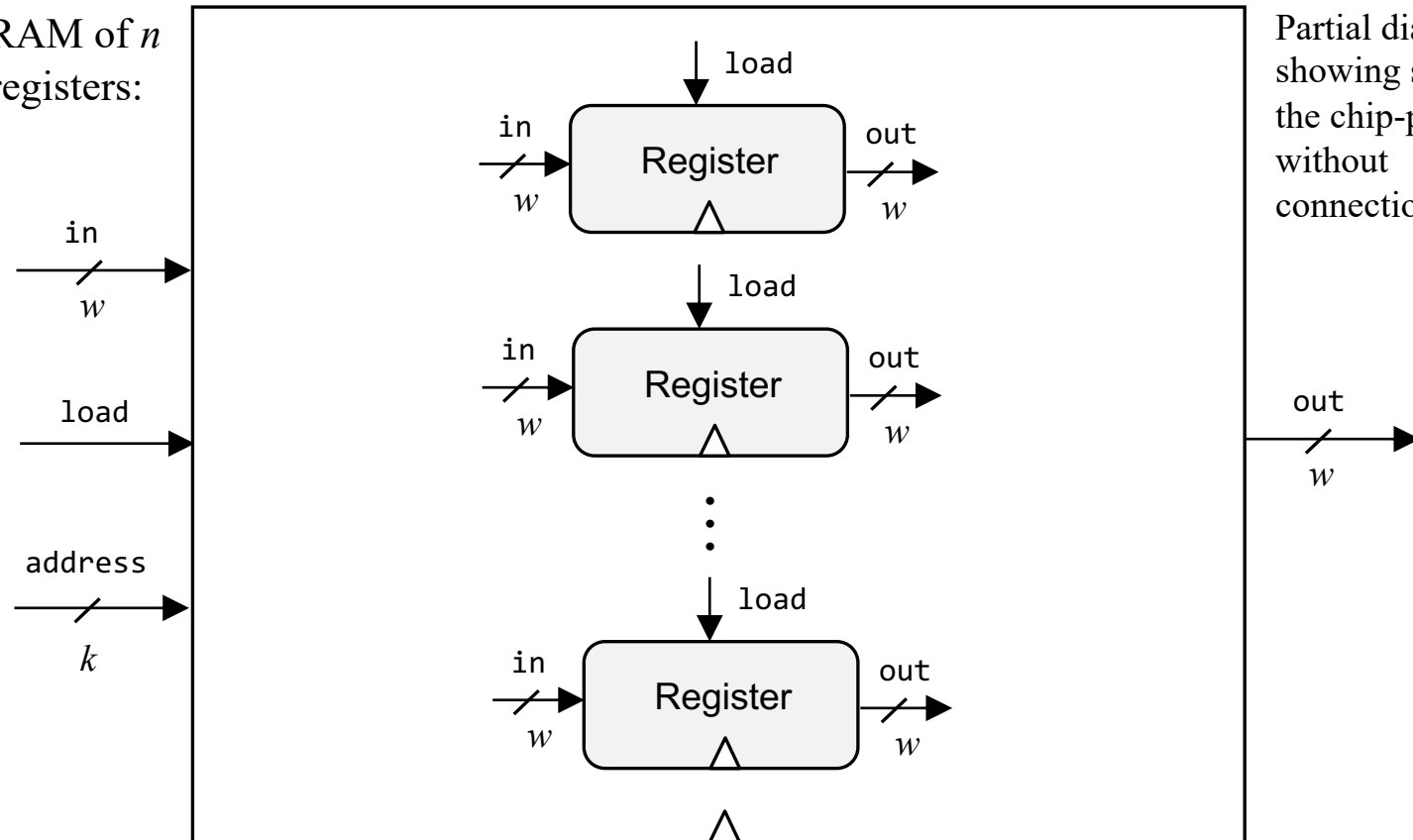

Partial diagram,
showing some of
the chip-parts,
without
connections

RAM: Implementation

RAM of n registers:

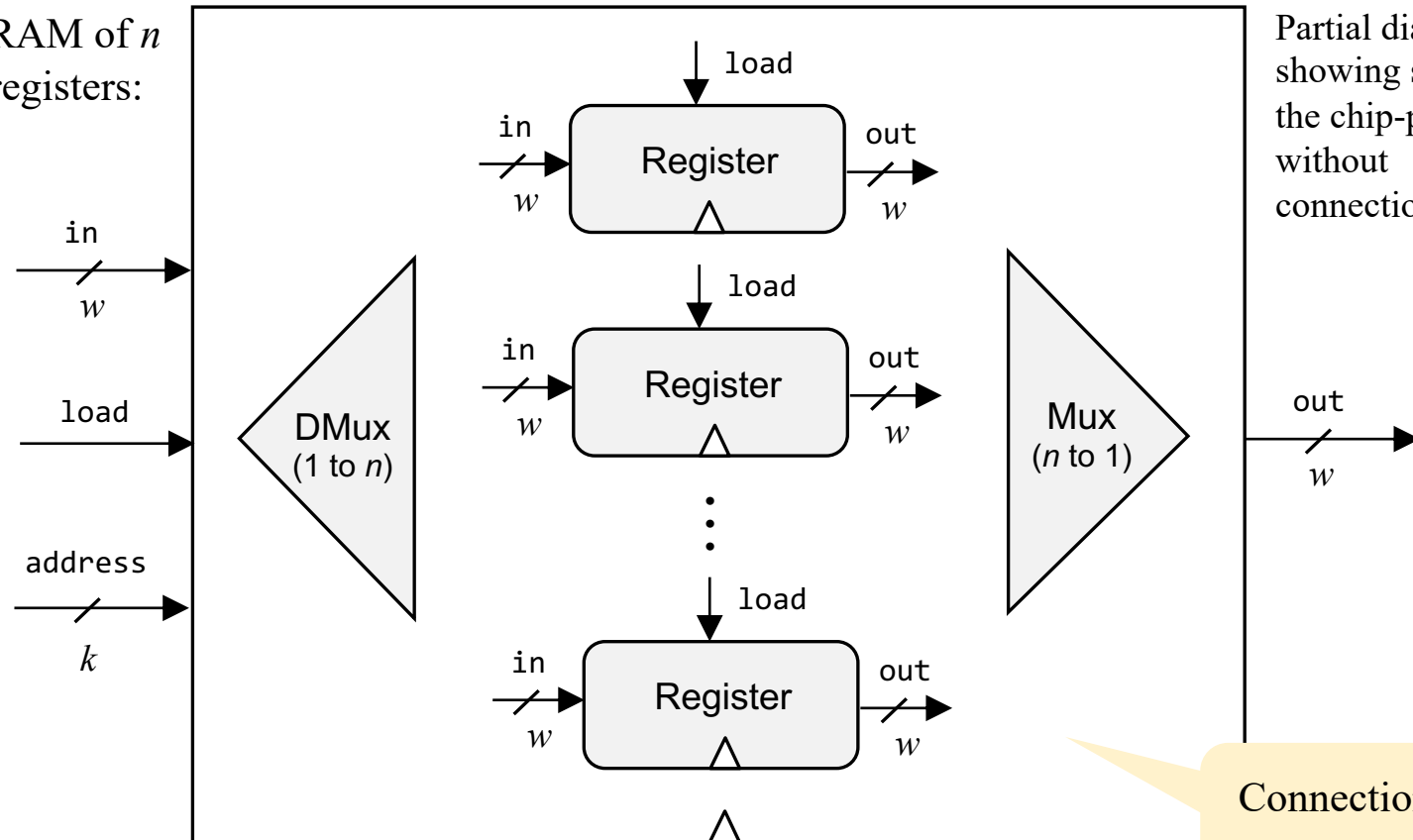


Partial diagram,
showing some of
the chip-parts,
without
connections

Connections?
You figure it out

Reading: Can be realized using a Mux

Writing: Can be realized using a DMux


RAM: Implementation

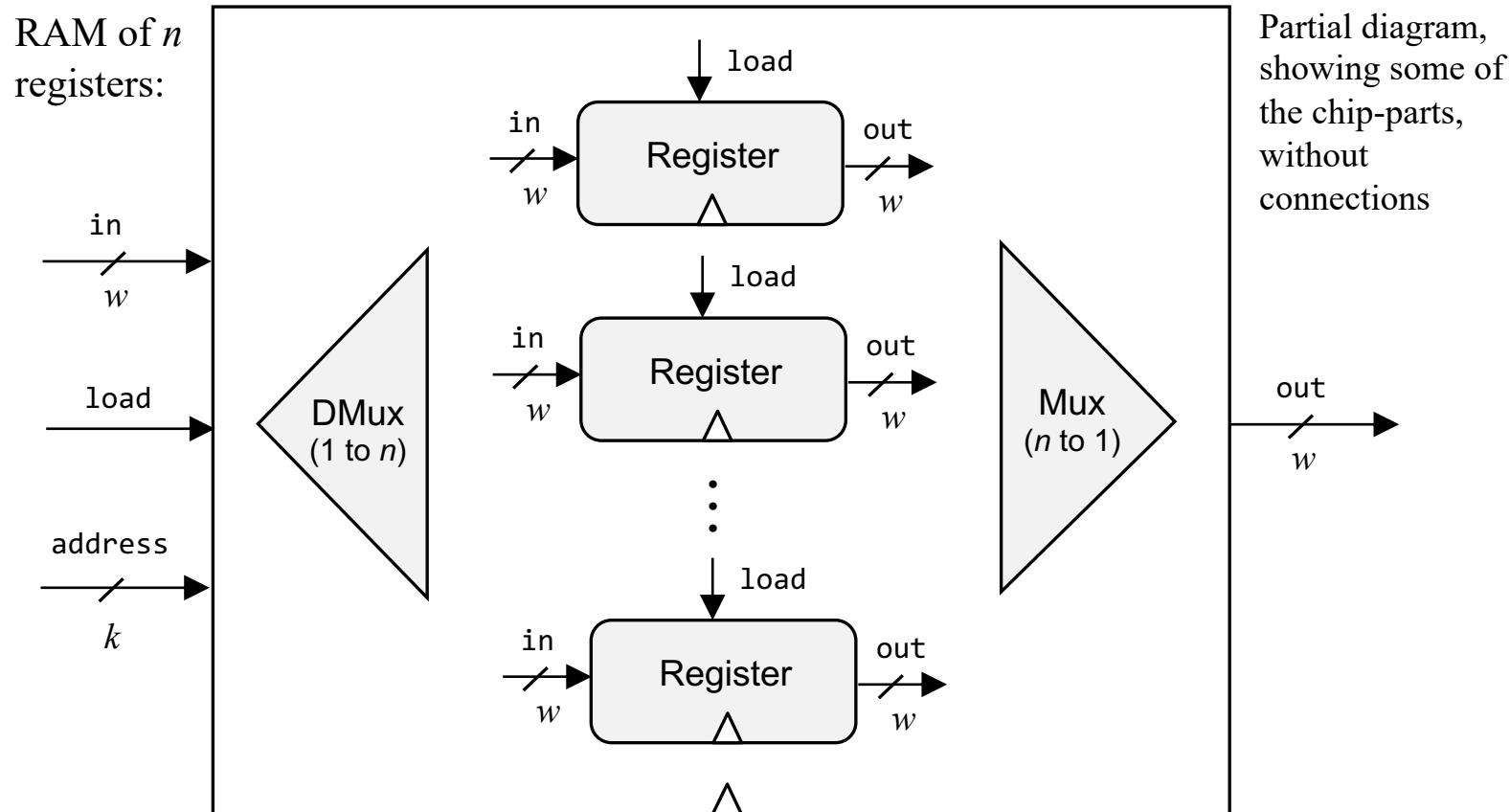


The RAM is a sequential logic chip:

- The direct access behavior is realized by the Mux / Dmux, which are combinational
- The storage behavior is realized by the registers, which are based on sequential logic.

RAM: Implementation

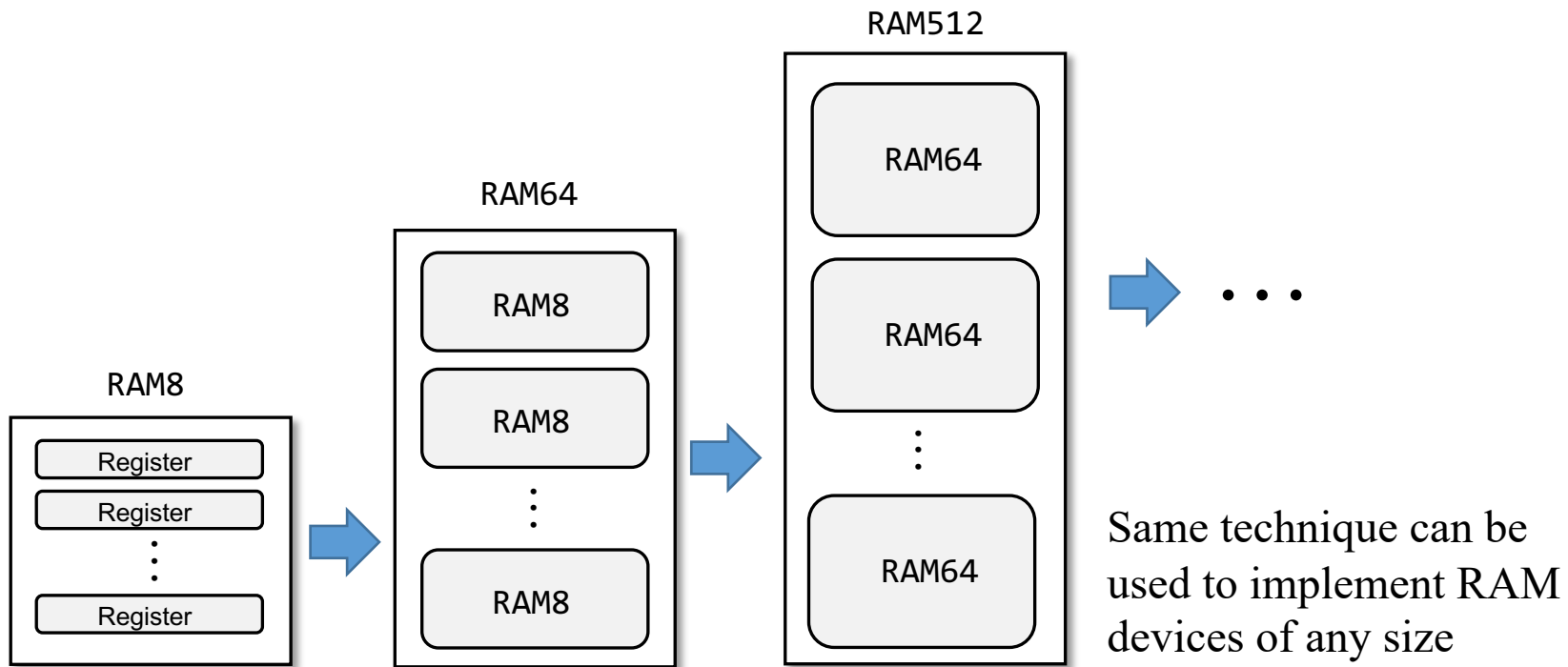

Hack RAM

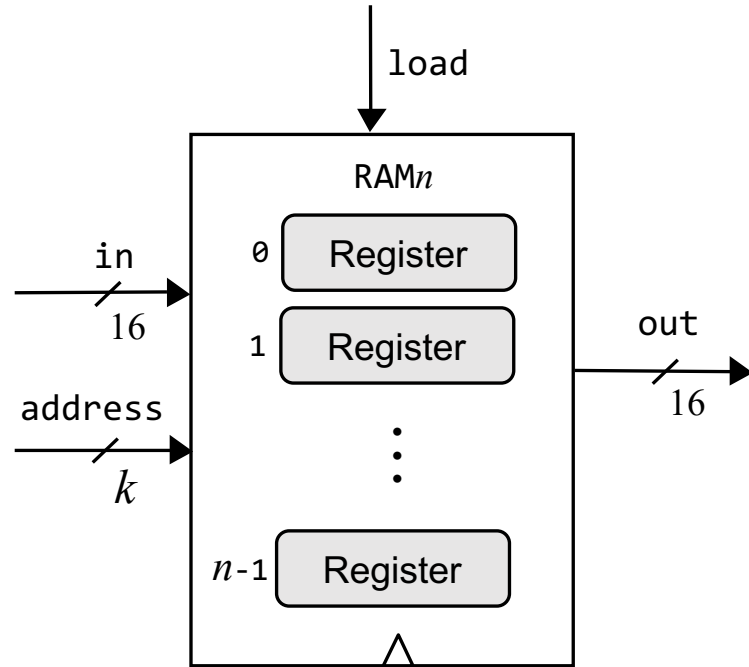

A family of 16-bit RAM chips:

chip name	n	k
RAM8	8	3
RAM64	64	6
RAM512	512	9
RAM4K	4096	12
RAM16K	16384	14

Why these particular RAM chips?

Because that's what we need for building the Hack computer.

Chapter 3: Memory

Abstraction

- Representing time
- Clock
- Registers
- RAM
- Counters

Implementation

- ✓ Data Flip Flop
- ✓ Registers
- ✓ RAM
- ➡ Project 3: Chips
 - Project 3: Guidelines

Project 3

Given:

- All the chips built in projects 1 and 2
- Data Flip-Flop (built-in DFF gate)

Why is the DFF built-in?

Build:

- Bit
- Register
- PC
- RAM8
- RAM64
- RAM512
- RAM4K
- RAM16K


DFF implementation

- The DFF gate logic implementation requires, among other things, connecting Nand gates with feedback loops
- The resulting implementation is elegant, yet impossible to realize on the supplied hardware simulator

The hardware simulator does not allow loops of combinational chips (like Nand)

- Instead, we use a built-in DFF implementation:
 
```
/** Data Flip-flop: out(t) = in(t-1)
 *  where t is the current time unit. */
CHIP DFF {
    IN in;
    OUT out;
    BUILTIN DFF;
    CLOCKED in;
}
```



Part of a possible
DFF implementation

Implementation notes:

We need the DFF as a chip-part in
one chip only: Bit

But... All the other memory chips
are built on top of it.

Project 3

Given:

- All the chips built in projects 1 and 2
- Data Flip-Flop (built-in DFF gate)


Build:



Bit

- Register
- PC
- RAM8
- RAM64
- RAM512
- RAM4K
- RAM16K

1-Bit register

 


Bit.hdl

```
/** 1-Bit register:
    if load(t) then out(t + 1) = in(t)
    else          out(t + 1) = out(t) */


CHIP Bit {
    IN in, load;
    OUT out;

    PARTS:
    // Put your code here:
}
```

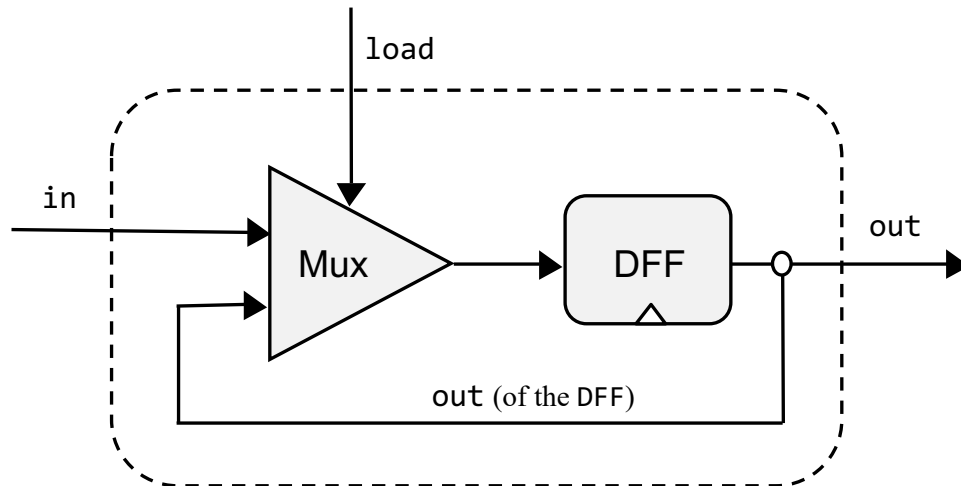

Implementation tip:
Follow the chip diagram

16-bit Register

 


Register.hdl

```
/** 16-bit register:
    if load(t) then out(t + 1) = in(t)
    else          out(t + 1) = out(t) */

CHIP Bit {
    IN in[16], load;
    OUT out[16];


    PARTS:
    // Put your code here:
}
```

 

Implementation tip:
Follow the chip diagram

Partial diagram, showing some of
the chip-parts, without connections

16-bit Counter

 

```
/**  
  A 16-bit counter.  
  if      reset(t) out(t + 1) = 0      // resetting  
  else if load(t)  out(t + 1) = in(t)   // setting  
  else if inc(t)   out(t + 1) = out(t) + 1 // incrementing  
  else            out(t + 1) = out(t)   // maintaining  
*/  
  
CHIP PC {  
  IN in[16], load, inc, reset;  
  OUT out[16];  
  PARTS:  
    // Put your code here:  
}
```

Implementation tip:

Can be built from a Register, an Incrementor, and Mux's

Project 3

Given

- All the chips built in projects 1 and 2
- Data Flip-Flop (built-in DFF gate)

Build the following chips

✓ Bit


✓ Register

✓ PC

➔ RAM8

- RAM64
- RAM512
- RAM4K
- RAM16K

8-Register RAM

 


RAM8.hdl

```
/* Memory of 8 registers, each 16 bit-wide.  
out holds the value stored at the memory location  
specified by address. If load==1, then the in value  
is loaded into the memory location specified by  
address (the loaded value will appear in out from  
the next time step onward).*/
```

```
CHIP RAM8 {  
    IN in[16], load, address[3];  
    OUT out[16];  
    PARTS:  
        // Put your code here:  
}
```

8-Register RAM

 

Partial diagram, showing some of the chip-parts, without connections

Implementation tip:

Follow the chip diagram, and figure out the missing connections.

Project 3

Given

- All the chips built in projects 1 and 2
- Data Flip-Flop (built-in DFF gate)

Build the following chips

✓ Bit

✓ Register

✓ PC

✓ RAM8

• RAM64


• RAM512

• RAM4K

• RAM16K

} A family of RAM chips

n -Register RAM

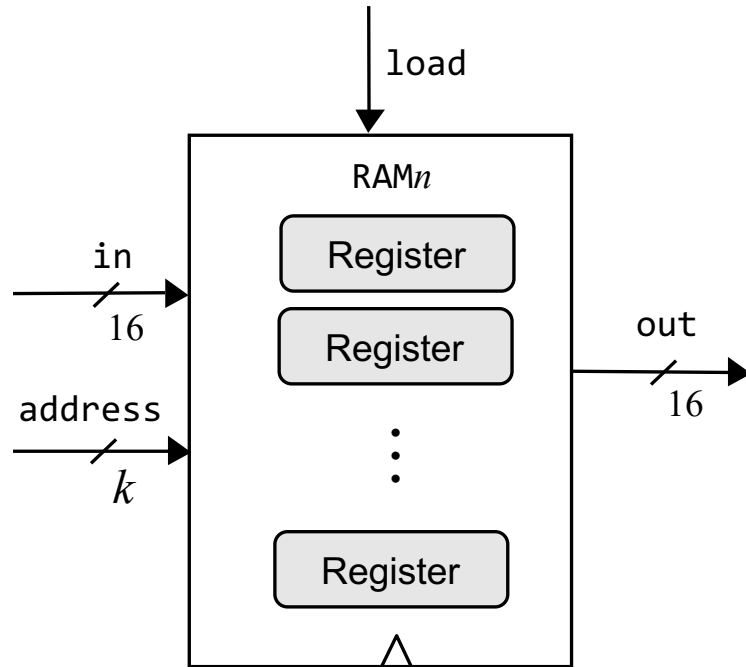


$RAM_n.hdl$

```
/* Memory of  $n$  registers, each 16 bit-wide.  
out holds the value stored at the memory location  
specified by address. If  $load==1$ , then the  $in$  value  
is loaded into the memory location specified by  
address (the loaded value will appear in  $out$  from  
the next time step onward).*/
```

```
CHIP  $RAM_n$  {  
    IN  $in[16]$ ,  $load$ ,  $address[k]$ ;  
    OUT  $out[16]$ ;  
    PARTS:  
        // Put your code here:  
}
```


n -Register RAM

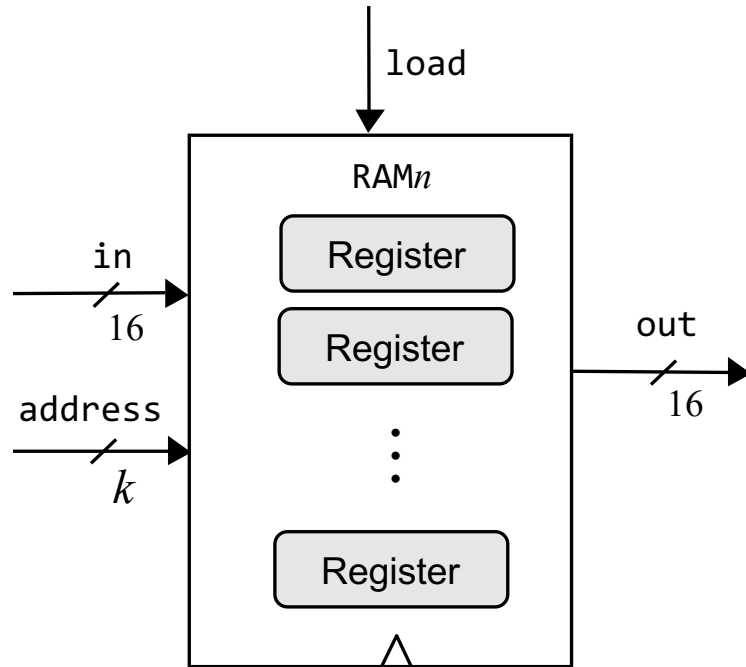

chip name	n	k
RAM8	8	3
RAM64	64	6
RAM512	512	9
RAM4K	4096	12
RAM16K	16384	14

Implementation tips

- Think about the RAM's address input as consisting of two fields:
 - One field selects a RAM-part;
 - The other field selects a register within that RAM-part
- Use logic gates to effect this logic.

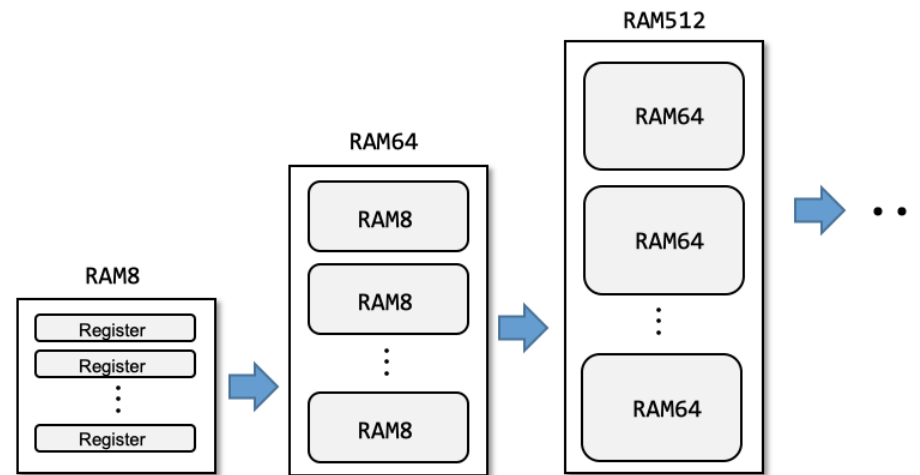






Chapter 3: Memory

Abstraction

- Representing time
- Clock
- Registers
- RAM
- Counters

Implementation

-  Data Flip Flop
-  Registers
-  RAM
-  Project 3: Chips
-  Project 3: Guidelines

Guidelines


- Implement the chips in the order in which they appear in the project guidelines
- If you don't implement some chips, you can still use their built-in implementations
- No need for “helper chips”: Implement / use only the chips we specified
- In each chip definition, strive to use as few chip-parts as possible
- You will have to use chips implemented in previous projects;
For efficiency and consistency's sake, use their built-in versions, rather than your own HDL implementations.

For technical reasons, the chips of project 3 are organized in two sub-folders named `projects/03/a` and `projects/03/b`


When writing and simulating the `.hdl` files, leave this folder structure as is.

That's It!
Go Do Project 3!

Nand to Tetris Roadmap: Hardware

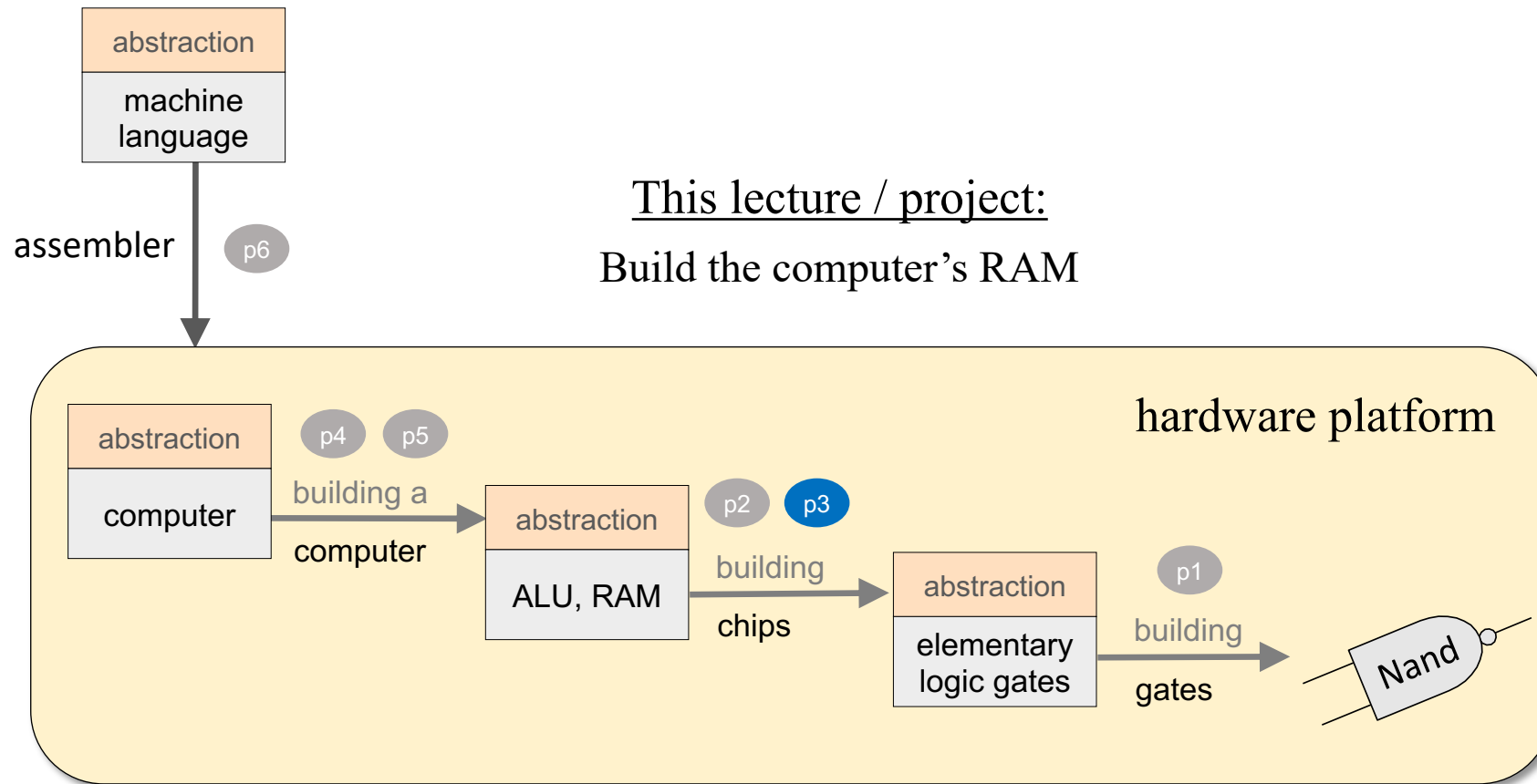

Nand to Tetris Roadmap: Hardware

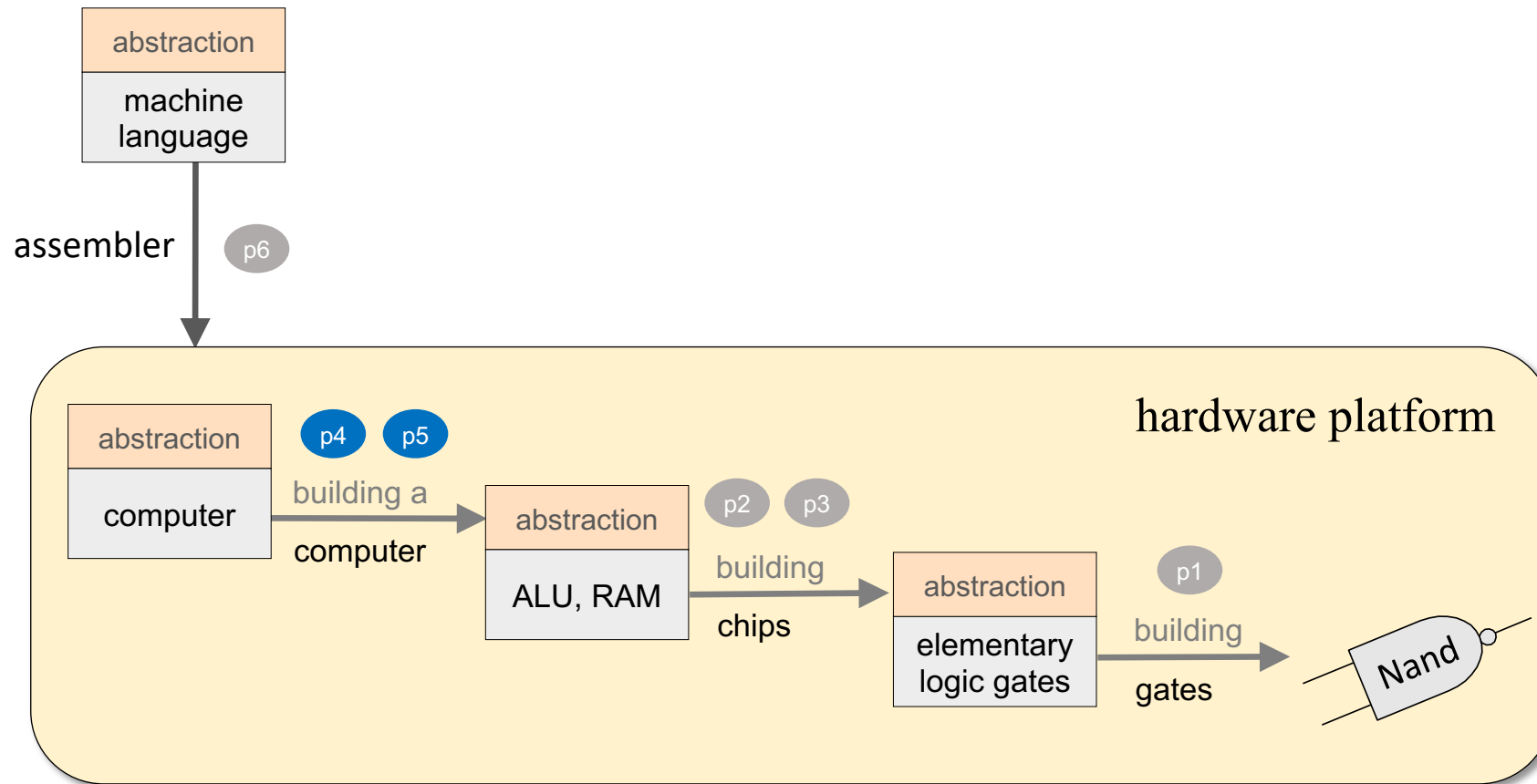

Next two lectures / projects:

- We'll build the computer (p5)
- But first, we'll get acquainted with its instruction set / machine language (p4).